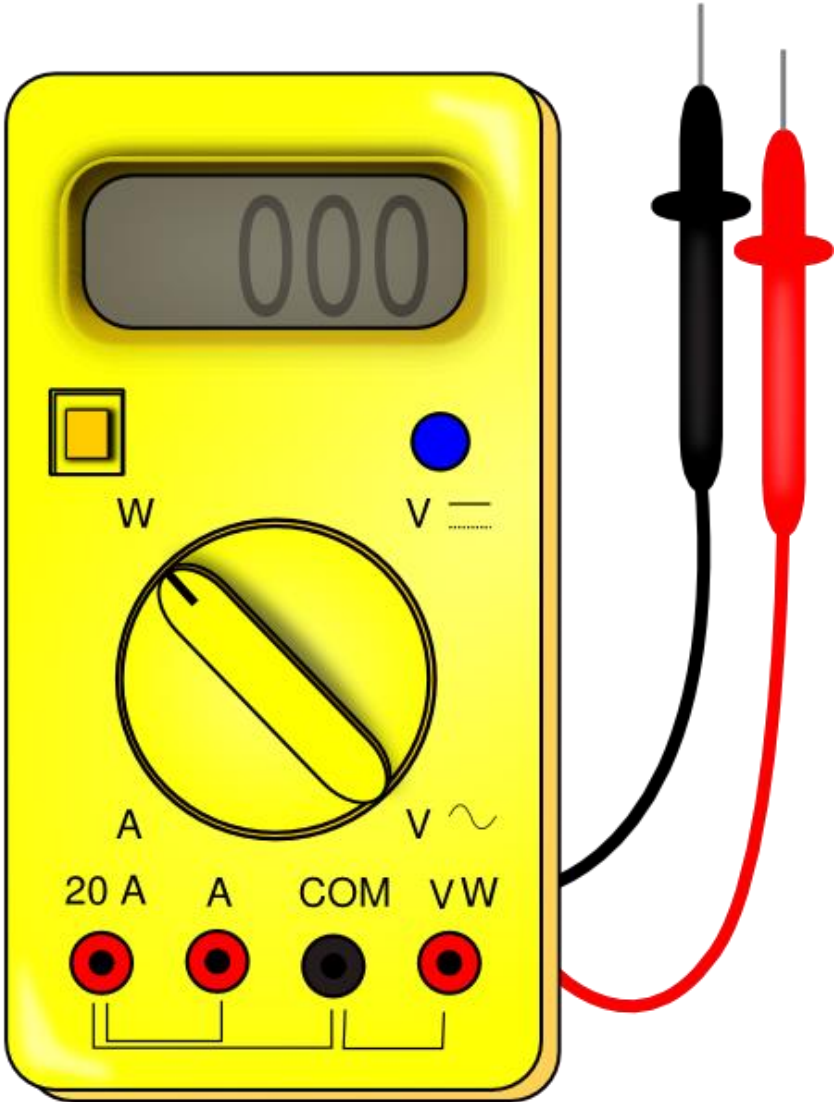




# Design Multimeters

Mingquan He | College of physics

# Multimeter




# Ammeter

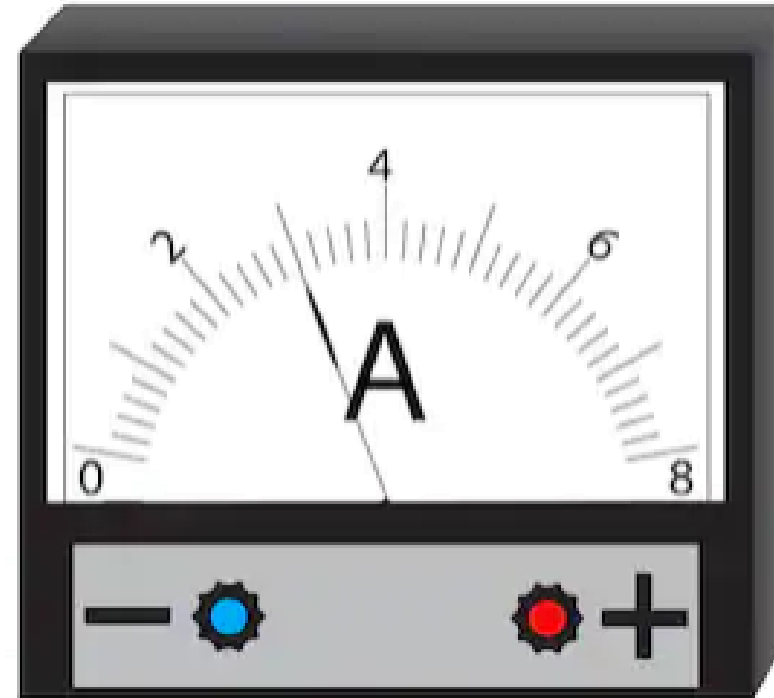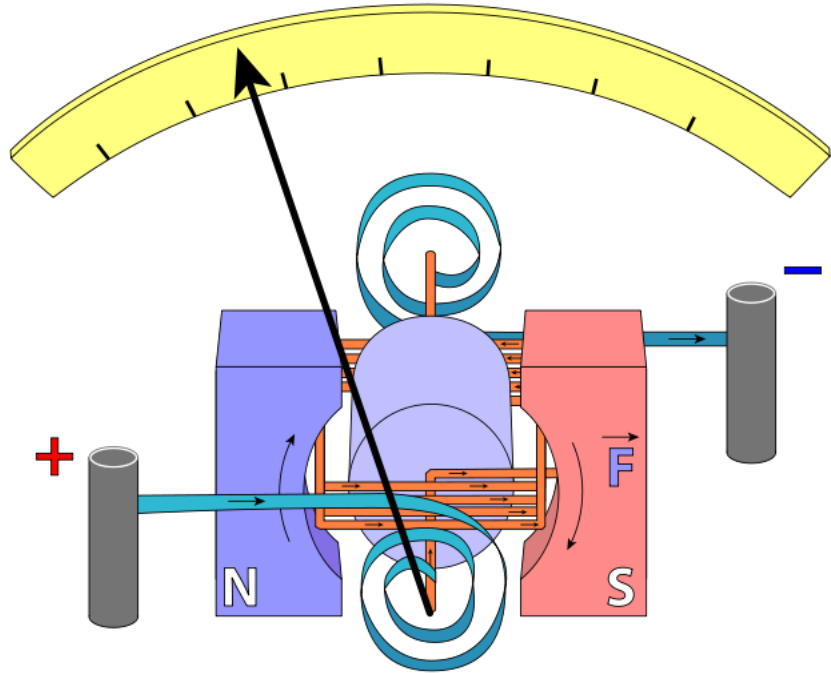

## Galvanometer


It is named after the Italian scientist [Luigi Galvani](#), who invented the frog galvanoscope.

# Design Multimeters based on an Ammeter

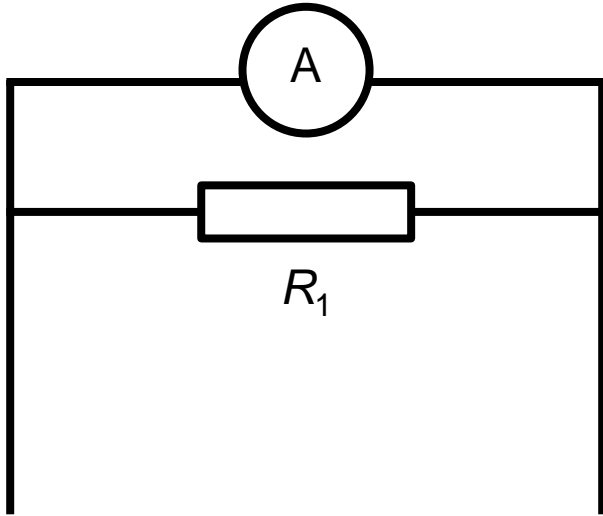


**In-parallel**

**Ammeter**

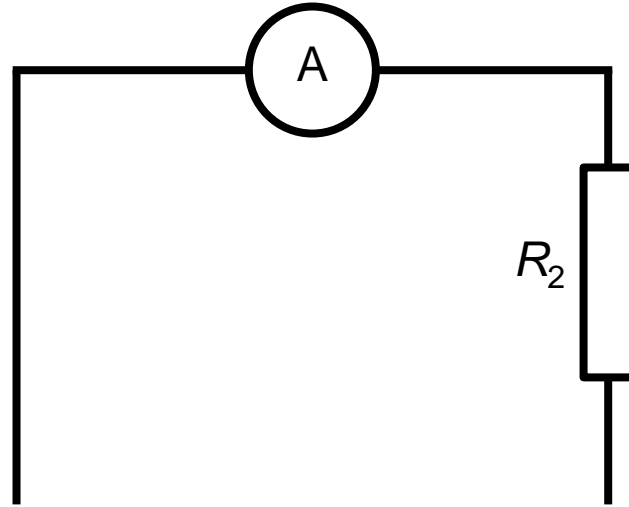

**In-series**

**Voltmeter**

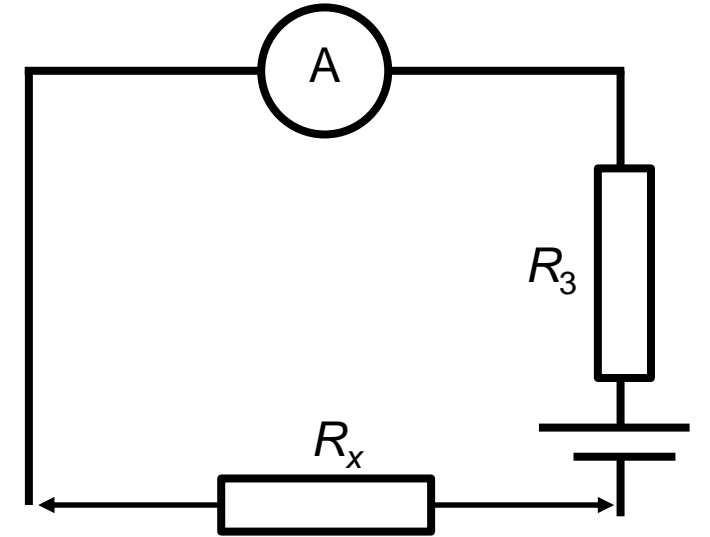


**In-series with a voltmeter**

**Ohmmeter**


**Task: determine  $R_1$ ,  $R_2$ ,  $R_3$**

# Internal Resistance of the Ammeter

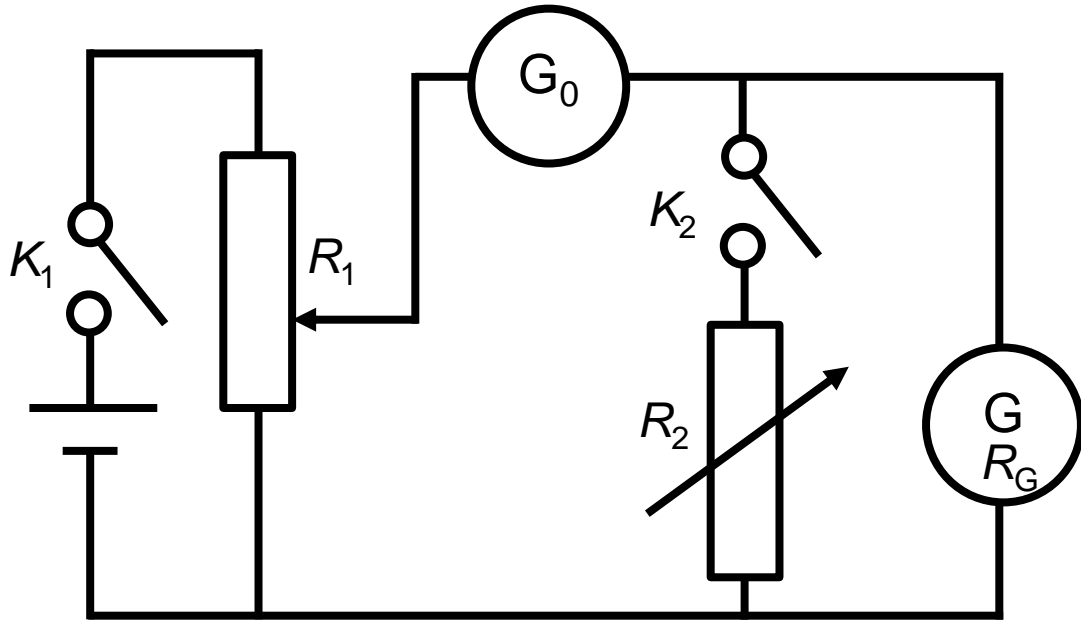

**Plan A**

**Half Value Method**

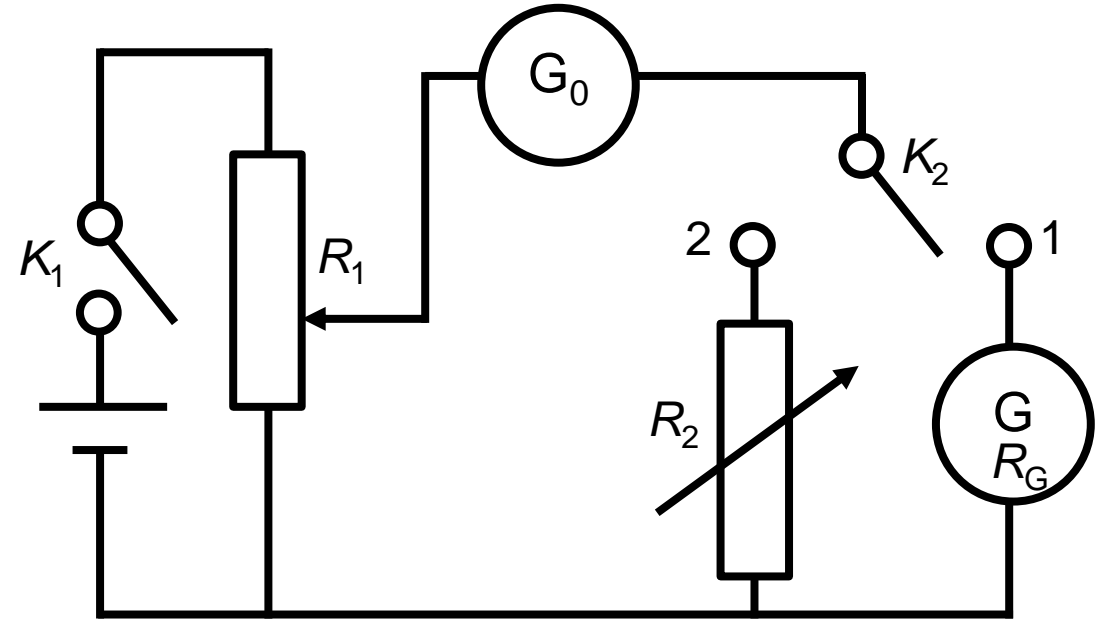

**Plan B**


**Replacement Method**

**The first step: determine the internal resistance of a given Ammeter.**

# Internal Resistance of the Ammeter





0.5 V

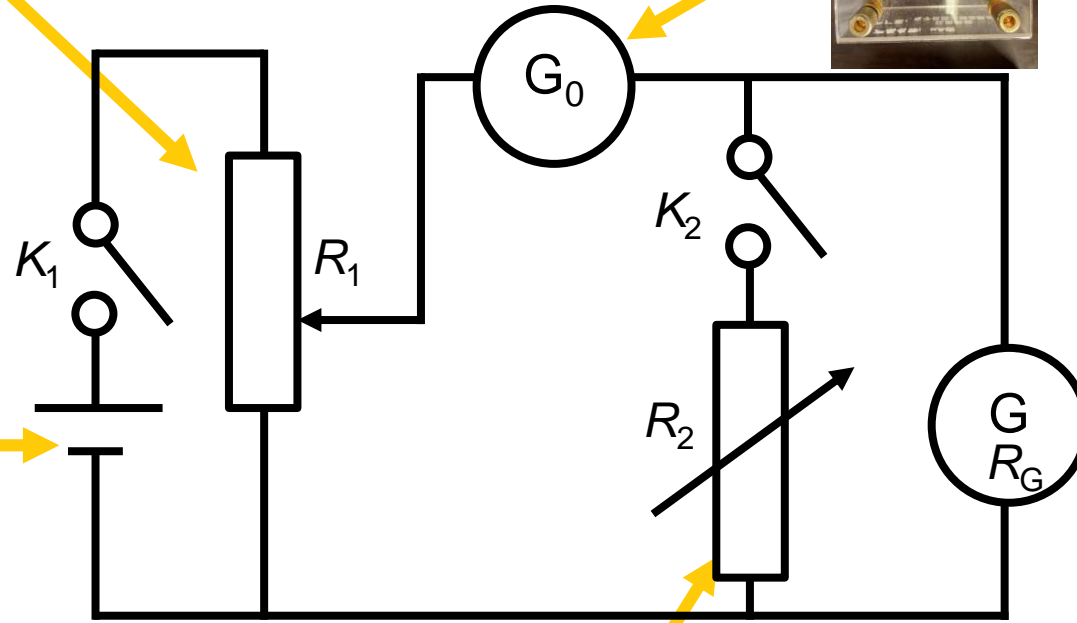

Plan A

Half Value Method

# Internal Resistance of the Ammeter

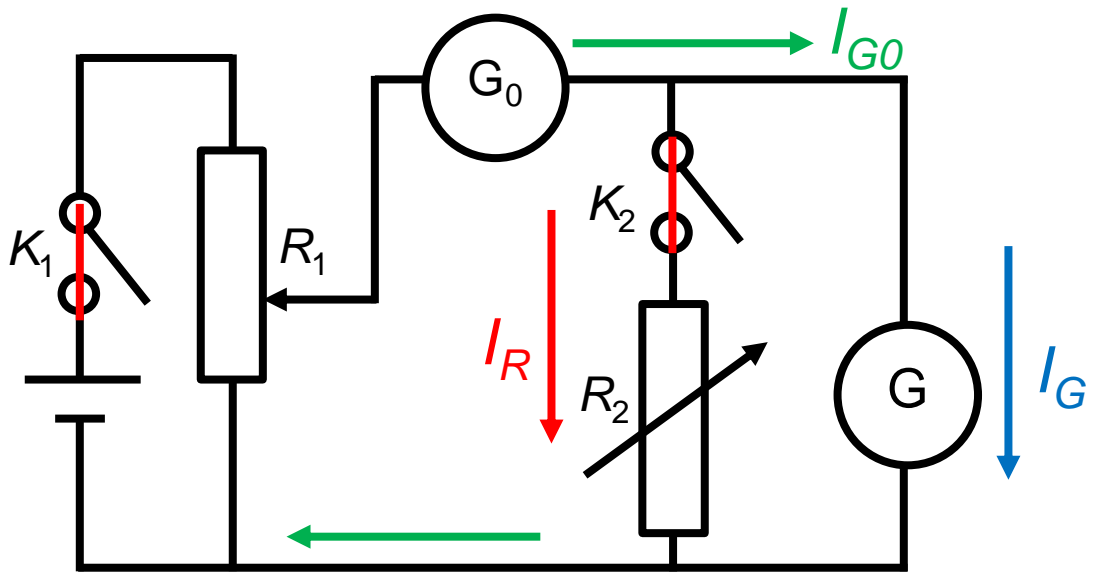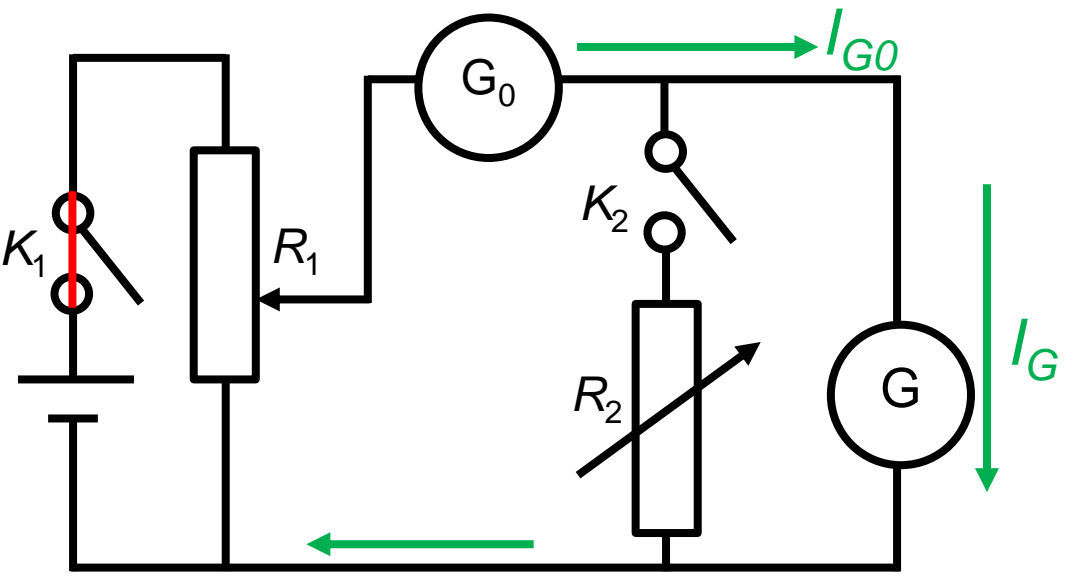

## Plan A Half Value Method

$R_1$ : sliding rheostat       $G_0$ : reference ammeter  
 $R_2$ : resistance box       $G$ : ammeter under test


### Step 1:

- $K_1$  ON  $K_2$  OFF       $G_0$  and  $G$  are in series
- Tune  $R_1$  and keep  $G$  at its full range       $I_{G0} = I_G$

### Step 2:

- $K_1$  ON  $K_2$  ON,  $R_2$  and  $G$  are in parallel
  - Tune  $R_1$  and  $R_2$  until       $I_G = I_{G0}/2$
  - Then one finds       $R_G = R_2$
- $R_G$ : the internal resistance of  $G$

# Internal Resistance of the Ammeter

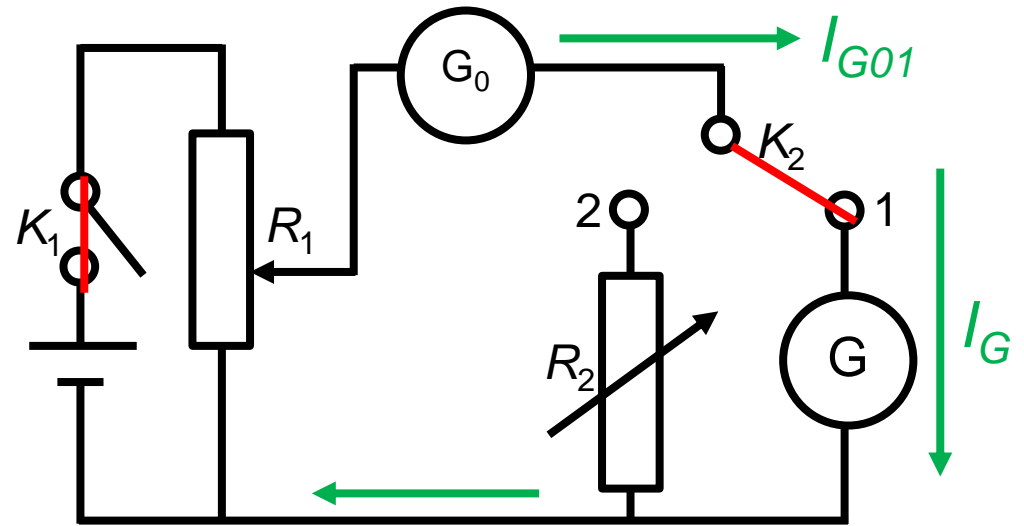


## Plan B Replacement Method

$R_1$ : sliding rheostat       $G_0$ : reference ammeter  
 $R_2$ : resistance box       $G$ : ammeter under test
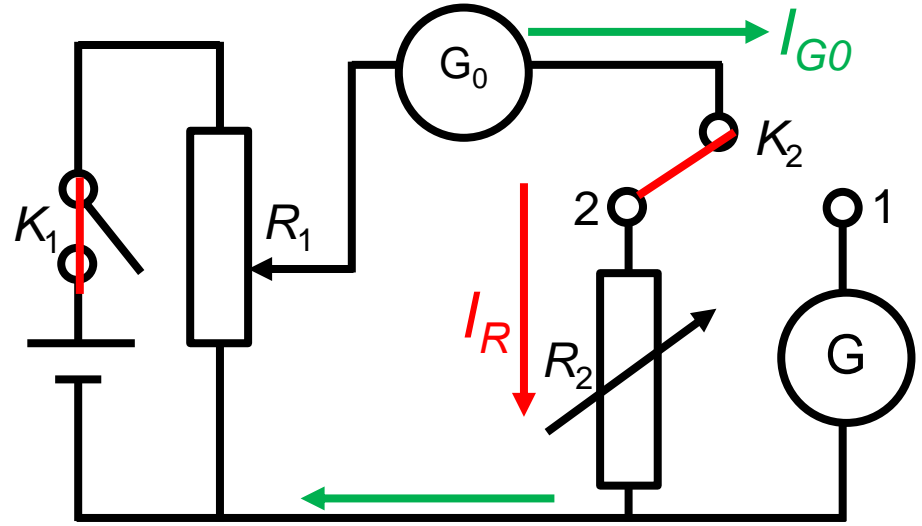
### Step 1:

- $K_1$  ON, Connect  $K_2$  to point 1  $G_0$  and  $G$  are in series
- Tune  $R_1$  and keep  $G$  at its full range  $I_{G01} = I_G$




### Step 2:

- $K_1$  ON, Connect  $K_2$  to point 2  $R_2$  and  $G_0$  are in series
- Keep  $R_1$  fixed and tune  $R_2$  until  $I_{G02} = I_{G01}$
- Then one finds  $R_G = R_2$

$R_G$ : the internal resistance of  $G$



# Design Ammeters and Voltmeters

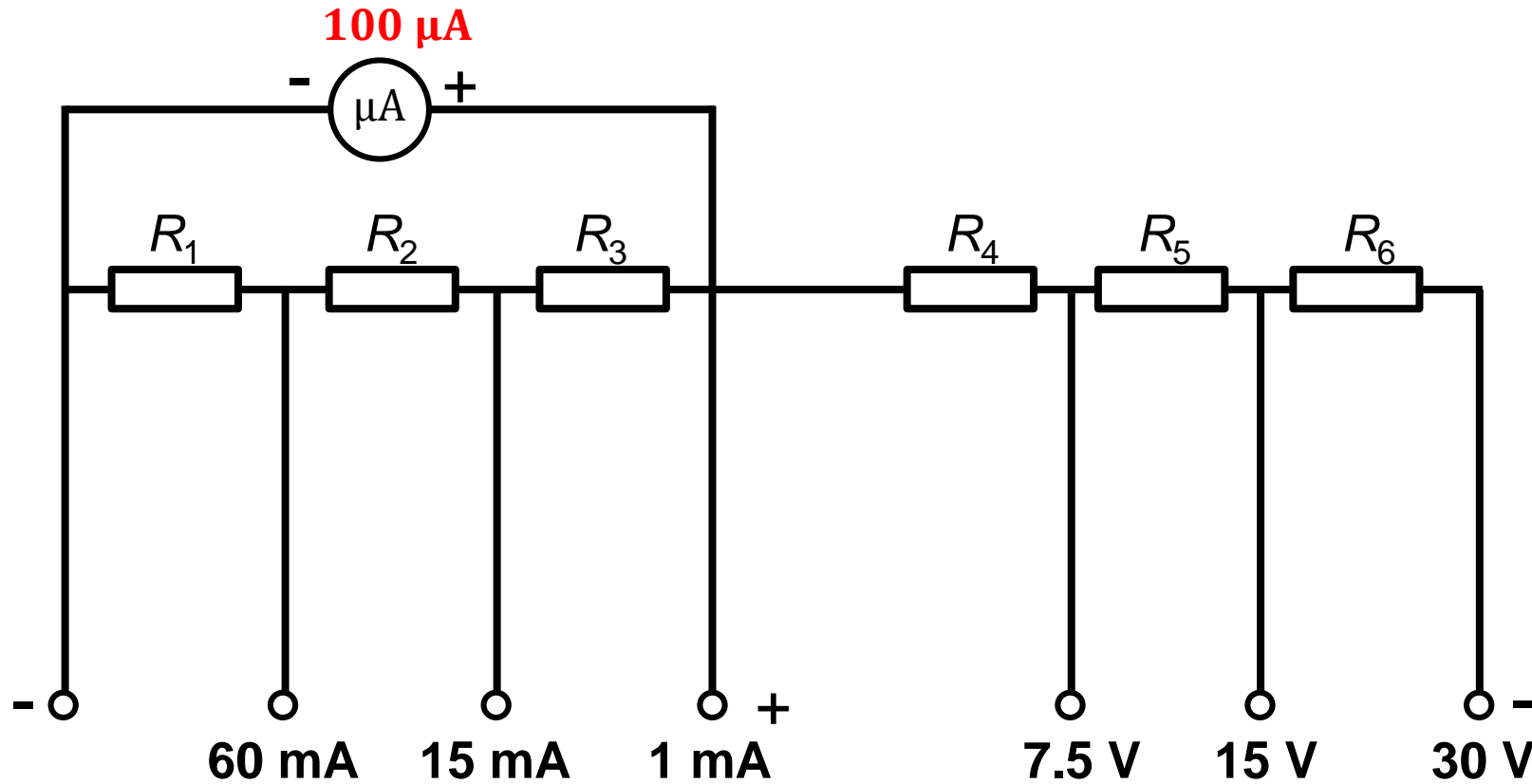


**Ammeter**


**Voltmeter**

$R_1 = 4.26\ \Omega$   
 $R_2 = 12.8\ \Omega$   
 $R_3 = 238\ \Omega$   
 $R_4 = 7.27\ \text{k}\Omega$   
 $R_5 = 7.5\ \text{k}\Omega$   
 $R_6 = 15\ \text{k}\Omega$

# Calibration of Ammeters and Voltmeters

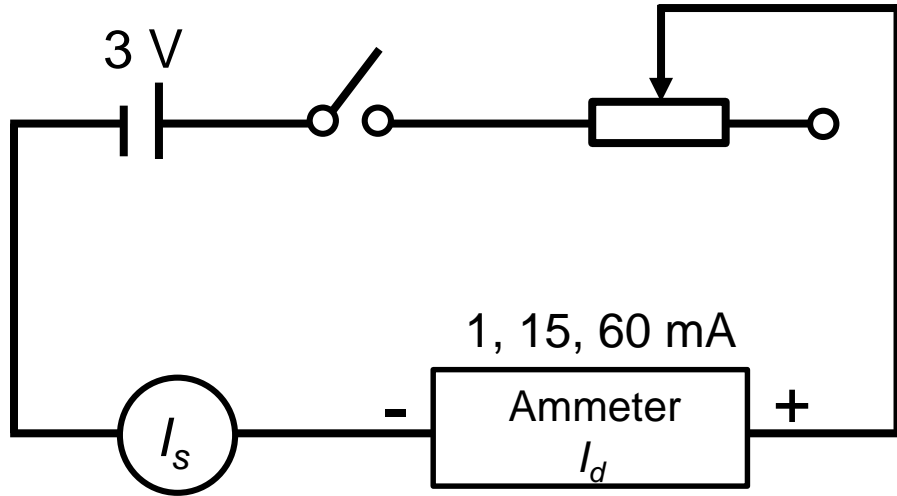


$I_d$ (mA)	$I_s$ (mA)	$\Delta I$ (mA)
1		
15		
60		

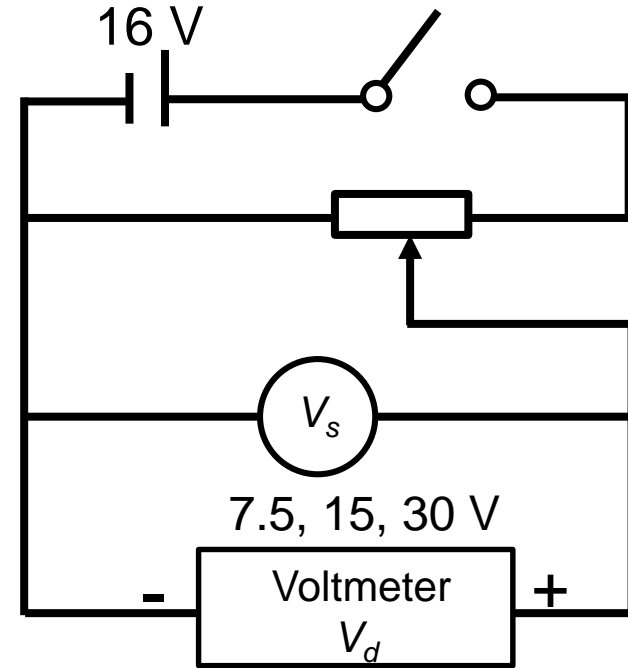

$V_d$ (V)	$V_s$ (V)	$\Delta V$ (V)
7.5		
15		
30		

# Design Multimeters

Time for fun!

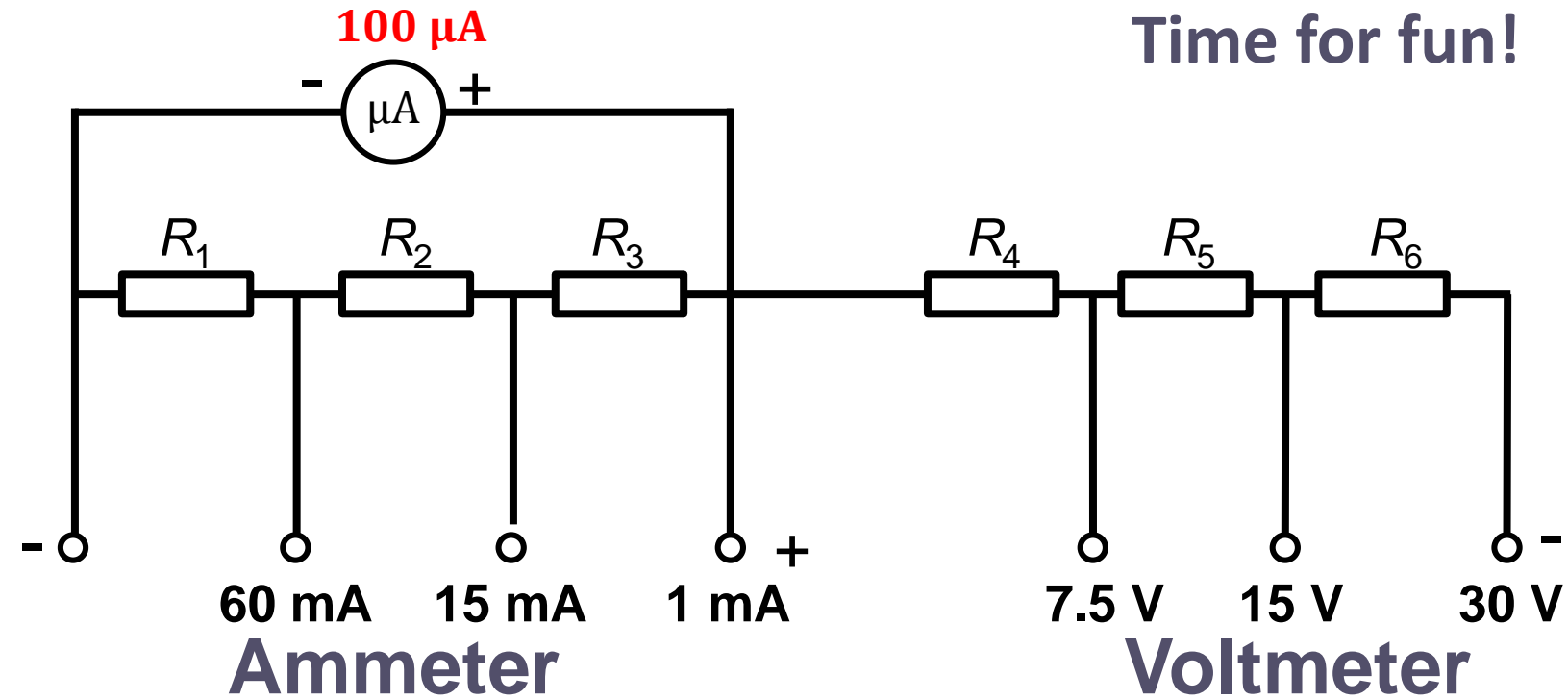

$$R_1 = 4.26 \Omega$$

$$R_2 = 12.8 \Omega$$

$$R_3 = 238 \Omega$$

$$R_4 = 7.27 \text{ k}\Omega$$

$$R_5 = 7.5 \text{ k}\Omega$$

$$R_6 = 15 \text{ k}\Omega$$

Appendix Table I: Experimental Raw Data for Multimeters

Internal Resistance of the Ammeter ( $\Omega$ )	$I_d$ (mA)	$I_s$ (mA)	$\Delta I$ (mA)	$V_d$ (V)	$V_s$ (V)	$\Delta V$ (V)
Half value method	1			7.5		
Replacement method	15			15		
Measured by multimeter	60			30		



| 何明全 |



mingquan.he@cqu.edu.cn



理科楼519

THANK YOU!