

Design a Digital Weighing Scale using Strain Gauges

Mingquan He | College of physics

Weighing Scale




Balance Scale



Digital Scale

What is a Strain Gauge?

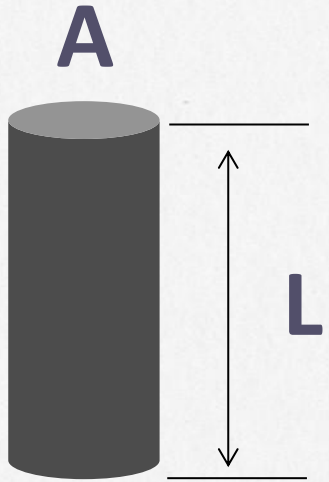

$$R = \rho \frac{L}{A}$$

R: Resistance
 ρ : Resistivity
L: Length
A: Area







$$\frac{\Delta R}{R} = k_m \frac{\Delta L}{L} = k_m \epsilon$$

k_m : Gauge factor
 $\epsilon = \frac{\Delta L}{L}$: Strain

ΔR is usually very small

Foil Strain Gauge

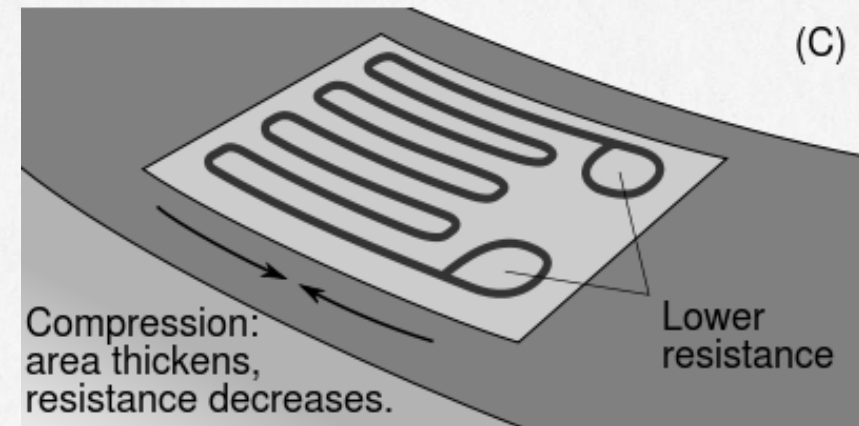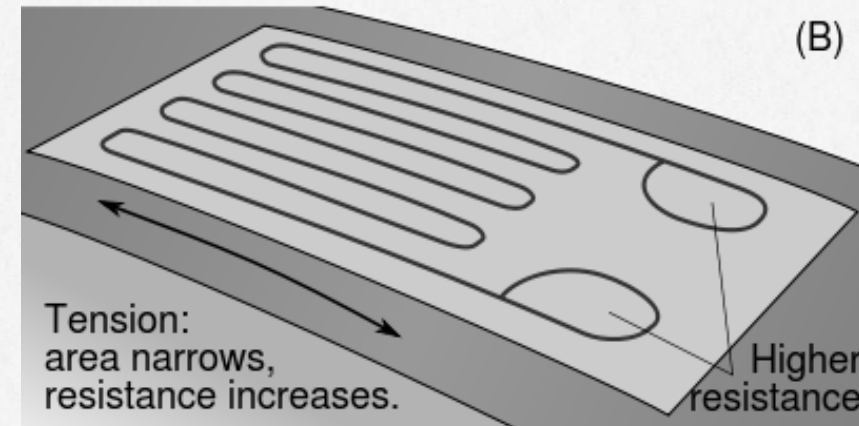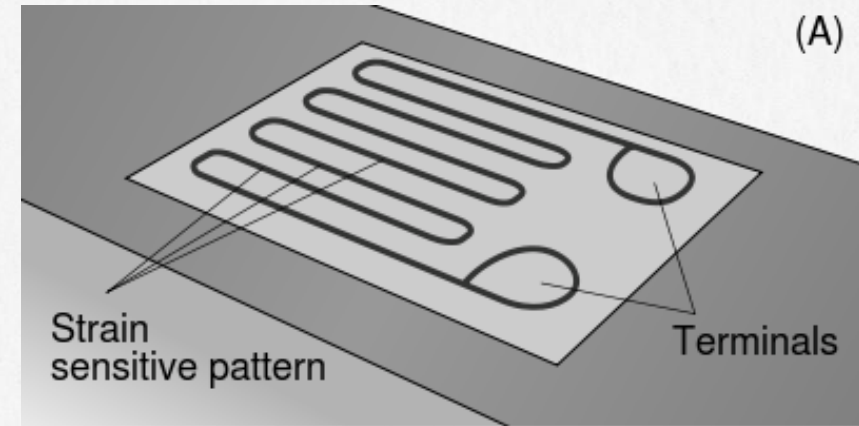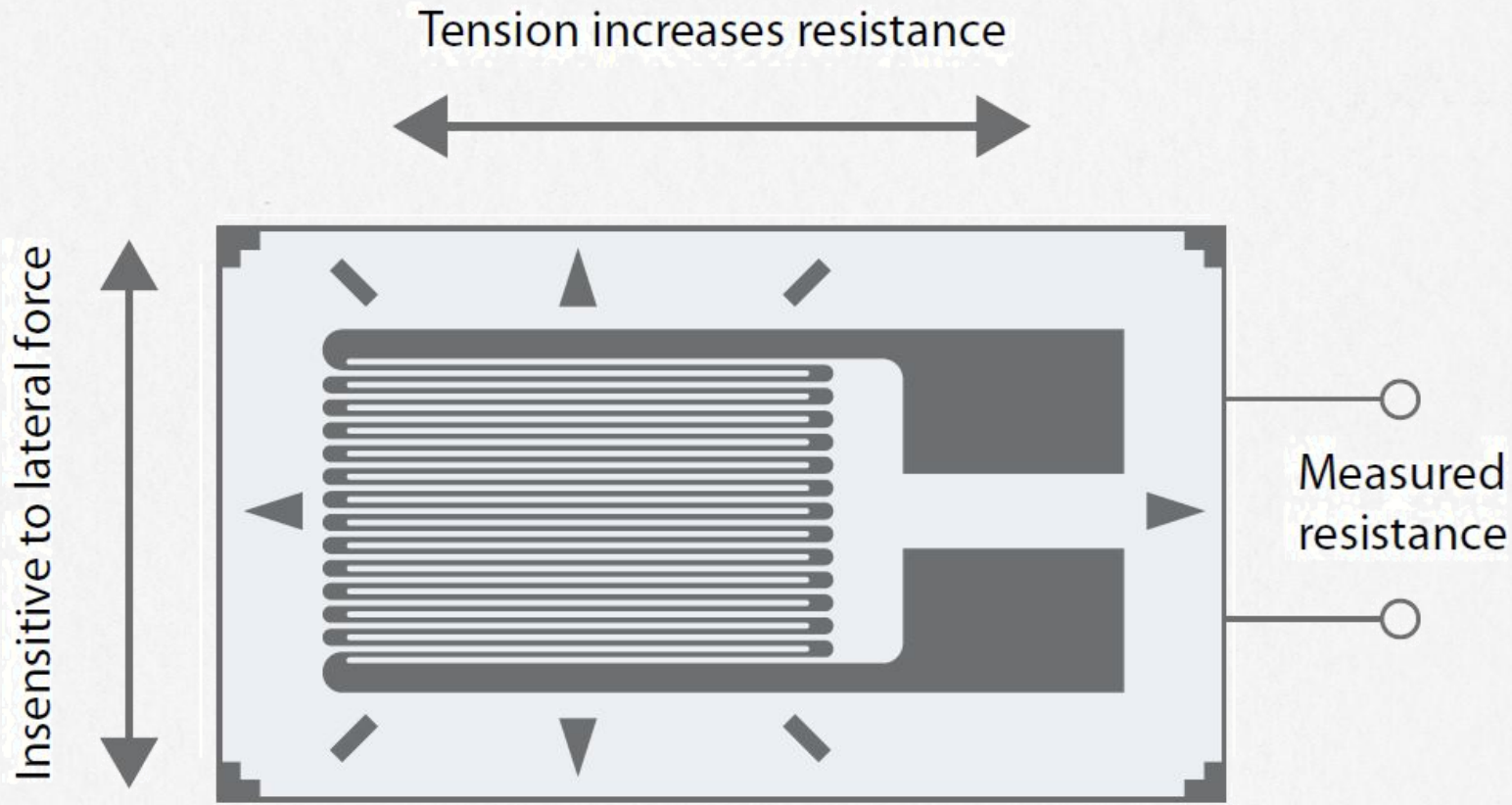

Why zigzag?

ΔR is usually very small


How to measure ΔR ?



Samuel Hunter Christie

Sir Charles Wheatstone

Wheatstone bridge

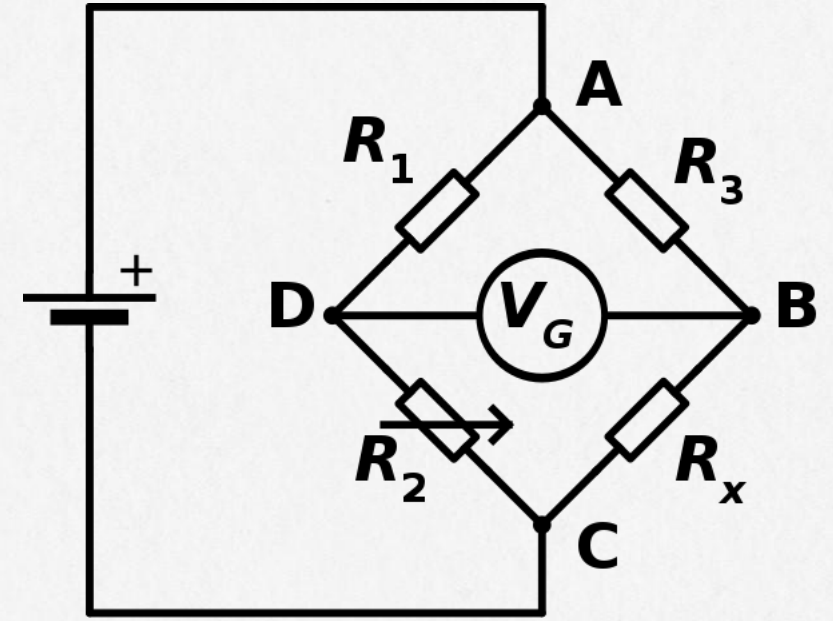


$$V_G = 0 \quad \frac{R_2}{R_1} = \frac{R_x}{R_3}$$

$$\text{Device Under Test (DUT): } R_x = R_3 \frac{R_2}{R_1}$$

ΔR is usually very small

How to measure ΔR ?

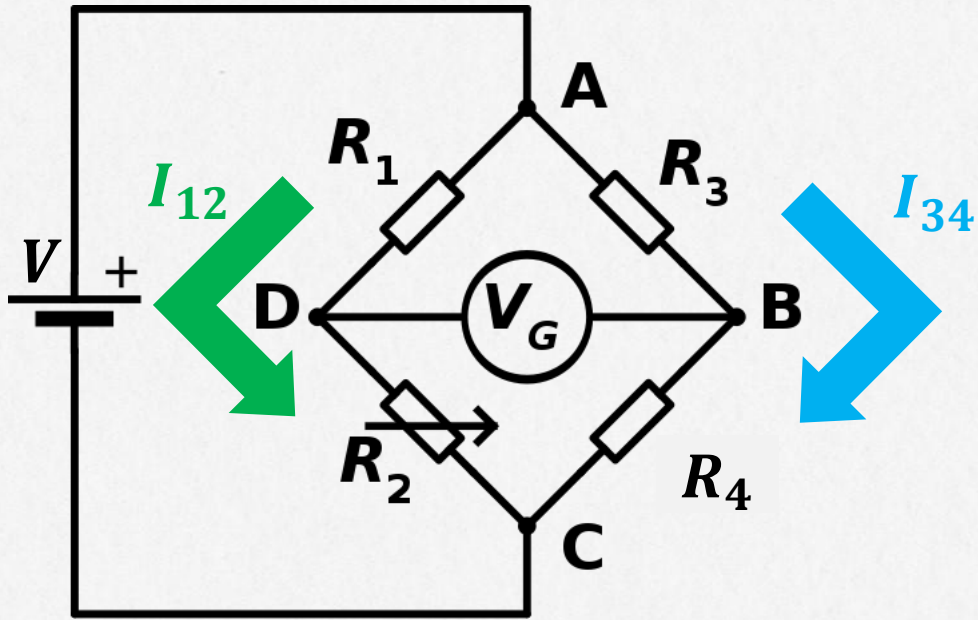


$$I_{12} = \frac{V}{R_1 + R_2} \quad I_{34} = \frac{V}{R_3 + R_4}$$

$$V_D - V_A = I_{12}R_1 = \frac{VR_1}{R_1 + R_2}$$

$$V_B - V_A = I_{34}R_3 = \frac{VR_3}{R_3 + R_4}$$

$$V_G = V_B - V_D = \frac{R_1R_4 - R_2R_3}{(R_1 + R_2)(R_3 + R_4)}$$

Quarter bridge

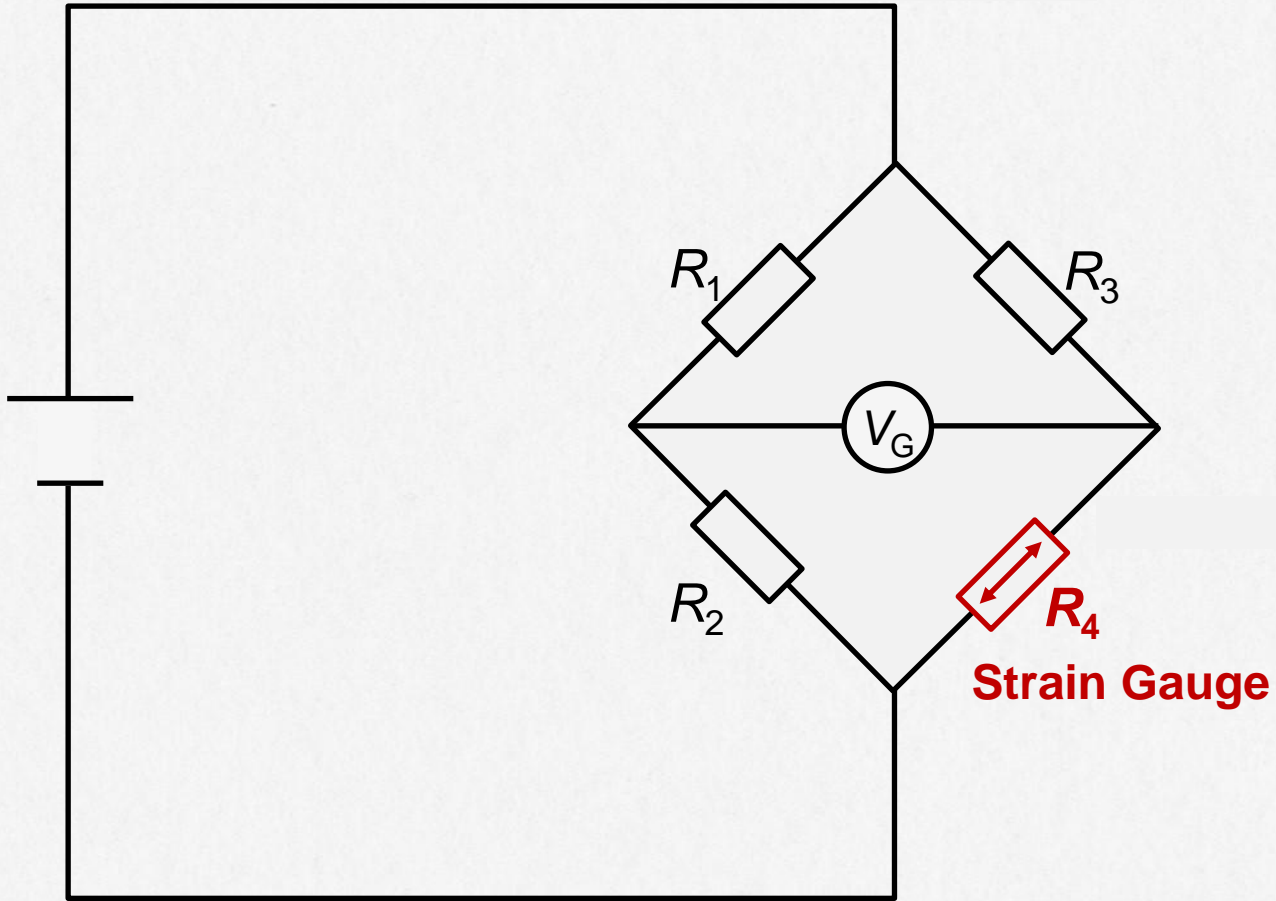


$$V_G = V_B - V_D = \frac{R_1 R_4 - R_2 R_3}{(R_1 + R_2)(R_3 + R_4)}$$

$$R_1 = R_2 = R_3 = R_4 = R$$

Apply strain $R_4 = R + \Delta R$

$$V_G = \frac{V \Delta R}{4 R}$$

Half bridge

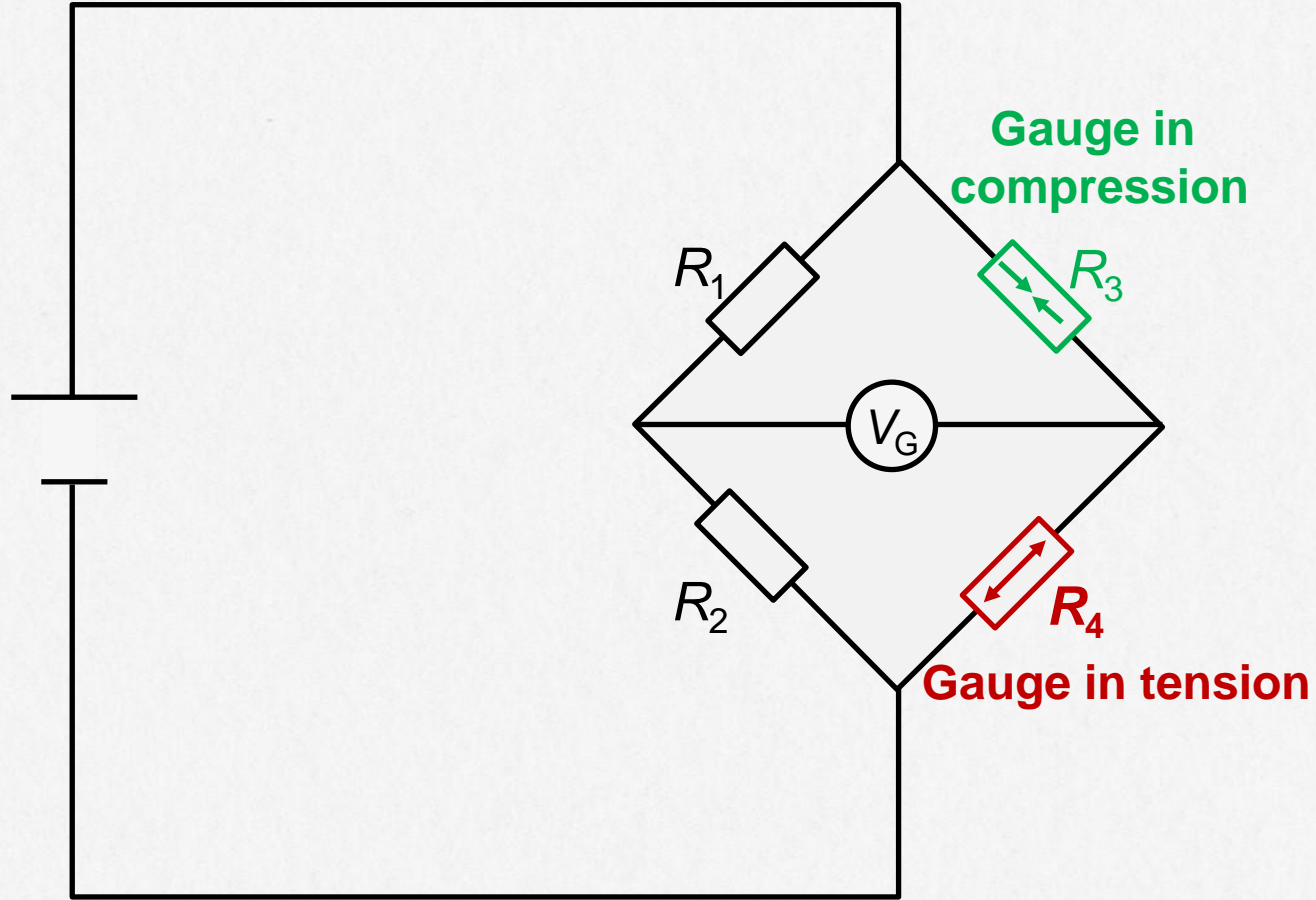

$$V_G = V_B - V_D = V \frac{R_1 R_4 - R_2 R_3}{(R_1 + R_2)(R_3 + R_4)}$$

$$R_1 = R_2 = R_3 = R_4 = R$$

Apply strain $R_3 = R - \Delta R$

$$R_4 = R + \Delta R$$

$$V_G = \frac{V \Delta R}{2 R}$$

Full bridge

ΔR **Same sign on cross arms!**
Opposite sign on neighboring arms !

$$V_G = V_B - V_D = \frac{R_1 R_4 - R_2 R_3}{(R_1 + R_2)(R_3 + R_4)}$$

$$R_1 = R_2 = R_3 = R_4 = R$$


Apply strain $R_1 = R + \Delta R$

$$R_2 = R - \Delta R$$


$$R_3 = R - \Delta R$$

$$R_4 = R + \Delta R$$


$$V_G = V \frac{\Delta R}{R}$$

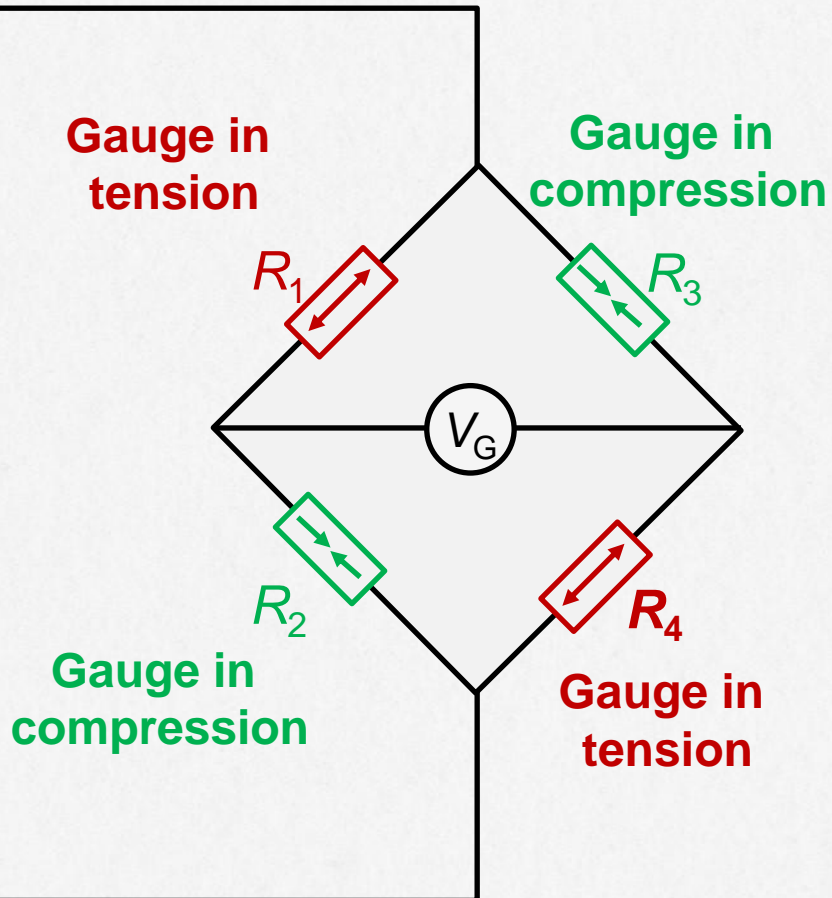



Experimental setup

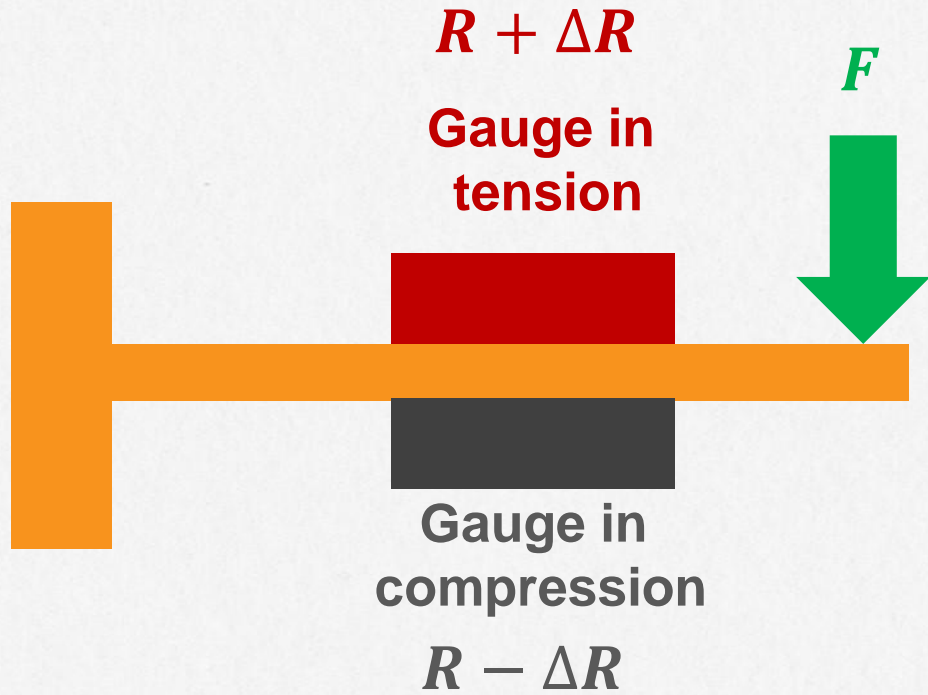

Cantilever

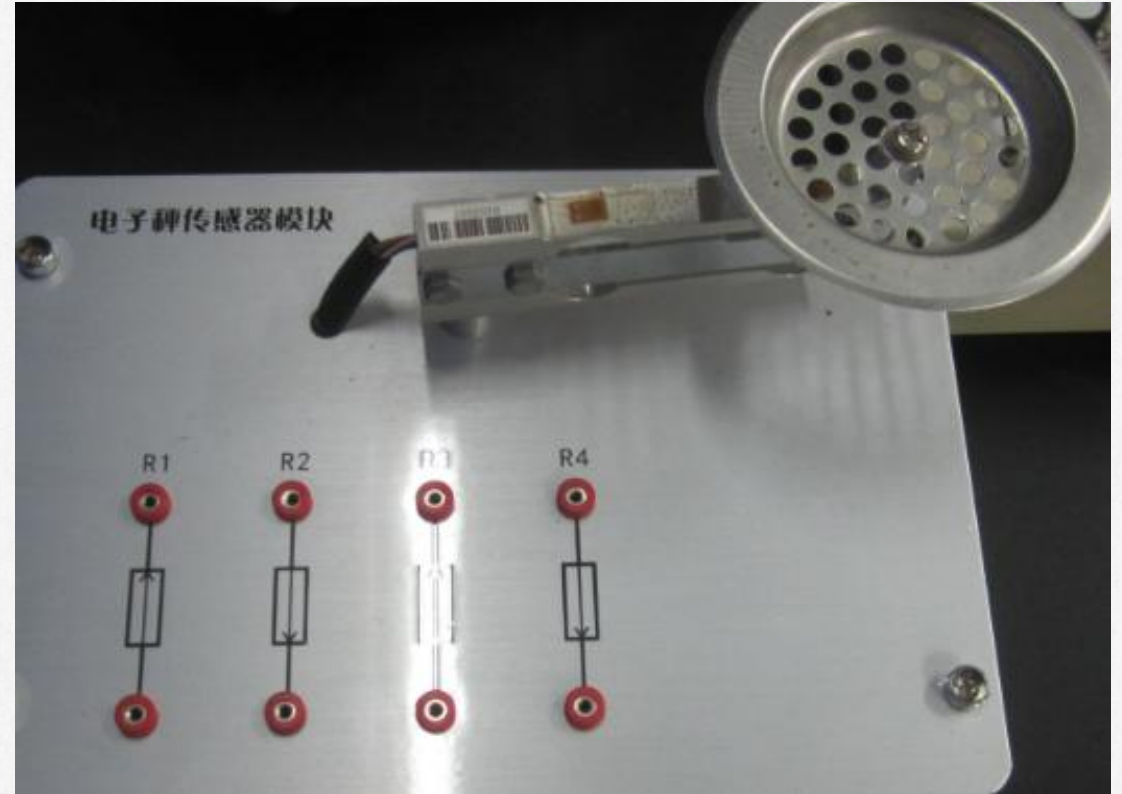

Bridge Circuit

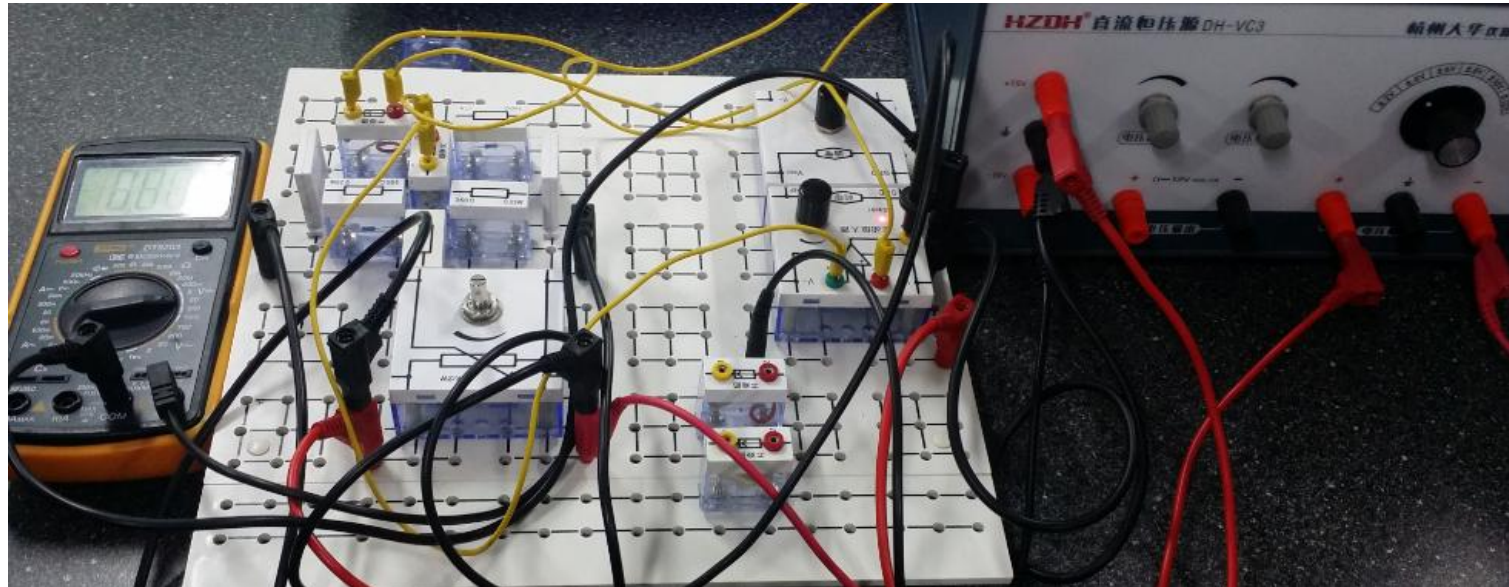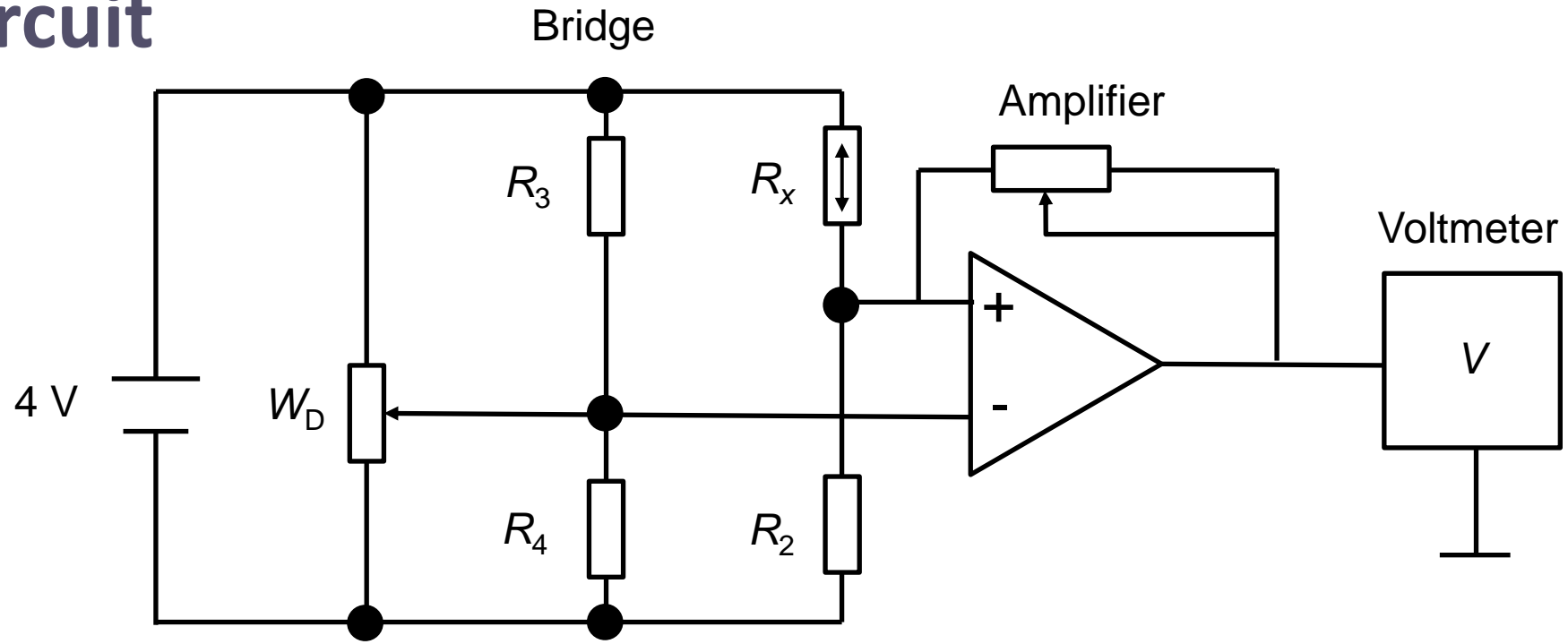

Design Digital Weighing Scale using Strain Gauges

Time for fun!

1.Safety

- Do not touch the output ends of the power supply directly.
- Do not short the two output ends of the power supply.
- Turn on the power supply only after the circuit is ready.

2.Data recording form




Appendix Table I: Experimental Raw Data

	Load(g)	V_1 (mV)	V_2 (mV)	V_3 (mV)	V_4 (mV)	V_5 (mV)	Mean V_G (mV)
Quarter Bridge							
Your Phone							

Data Analysis

Weighing scale calibration curve

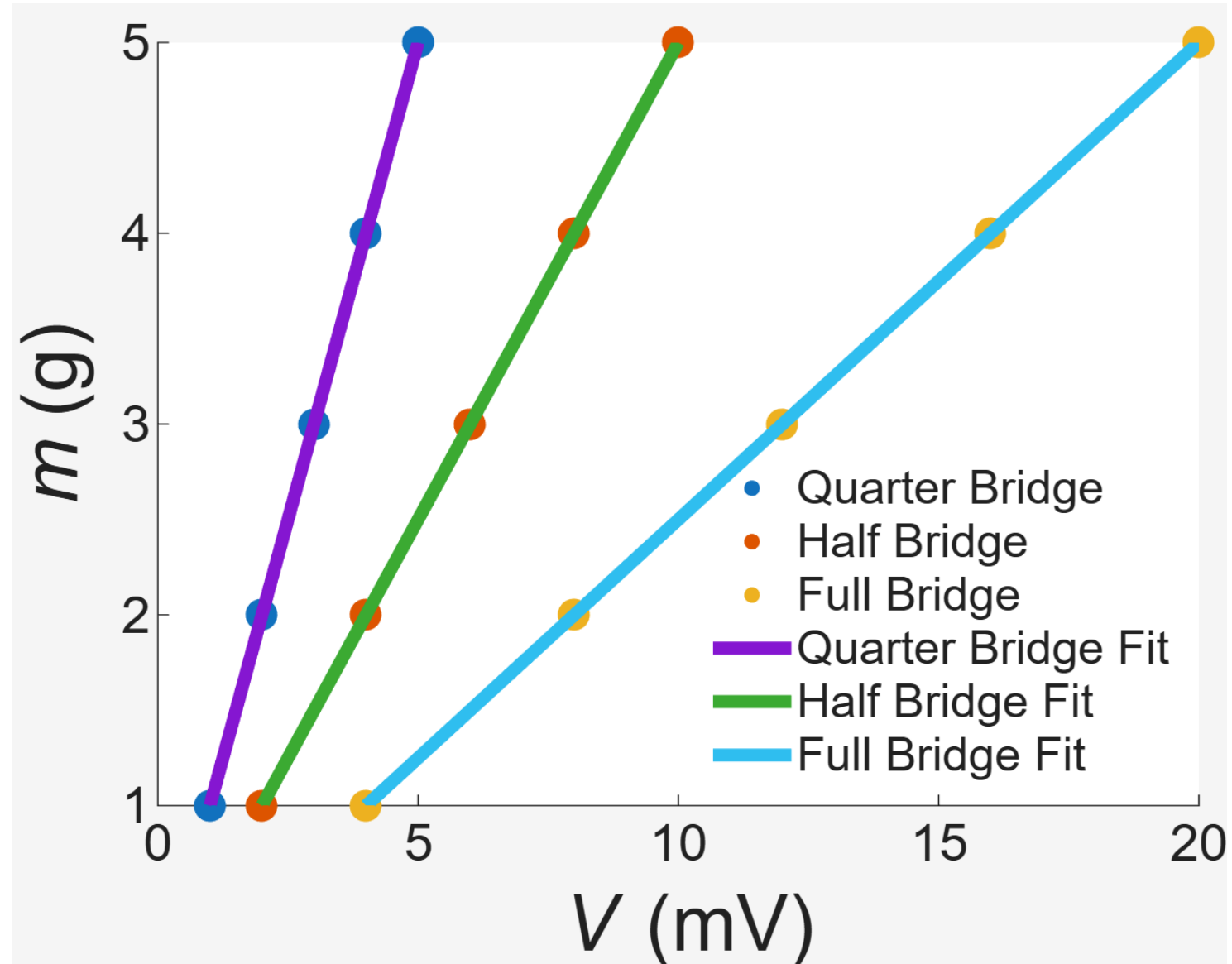

Data Analysis

```
m=[1,2,3,4,5]; %砝码质量, 单位g
Vq=[1,2,3,4,5]; %quarter bridge电压读数,单位是mV
Vh=[2,4,6,8,10]; %half bridge电压读数,单位是mV
Vf=[4,8,12,16,20]; %full bridge电压读数,单位是mV
pq=polyfit(Vq,m,1); %quarter bridge线性拟合, pq(1)是斜率
fitq=polyval(pq,Vq); %计算quarter bridge拟合数据
ph=polyfit(Vh,m,1); %half bridge线性拟合, ph(1)是斜率
fith=polyval(ph,Vh); %计算half bridge拟合数据
pf=polyfit(Vf,m,1); %half bridge线性拟合, ph(1)是斜率
fitf=polyval(pf,Vf); %计算full bridge拟合数据
figure; %开始画图
scatter(Vq,m,150,'filled','DisplayName','Quarter Bridge'); %画quarter bridge原始数据散点
hold on;
scatter(Vh,m,150,'filled','DisplayName','Half Bridge'); %画half bridge原始数据散点
hold on;
scatter(Vf,m,150,'filled','DisplayName','Full Bridge'); %画full bridge原始数据散点
hold on; %不关图, 后面还要画拟合线
plot(Vq,fitq,'LineWidth',5,'DisplayName','Quarter Bridge Fit'); %画拟合线
plot(Vh,fith,'LineWidth',5,'DisplayName','Half Bridge Fit'); %画拟合线
plot(Vf,fitf,'LineWidth',5,'DisplayName','Full Bridge Fit'); %画拟合线
set(gca,'FontName','Arial','FontSize',20); %设置图横纵坐标的字体大小
xlabel('{\it V} (mV)','FontSize',30); %设置横坐标label及字体大小
ylabel('{\it m} (g)','FontSize',30); %设置纵坐标label及字体大小
legend('Location','southeast');%画图标位置
legend('boxoff')
hold off
```



| 何明全 |



mingquan.he@cqu.edu.cn



理科楼519

THANK YOU!